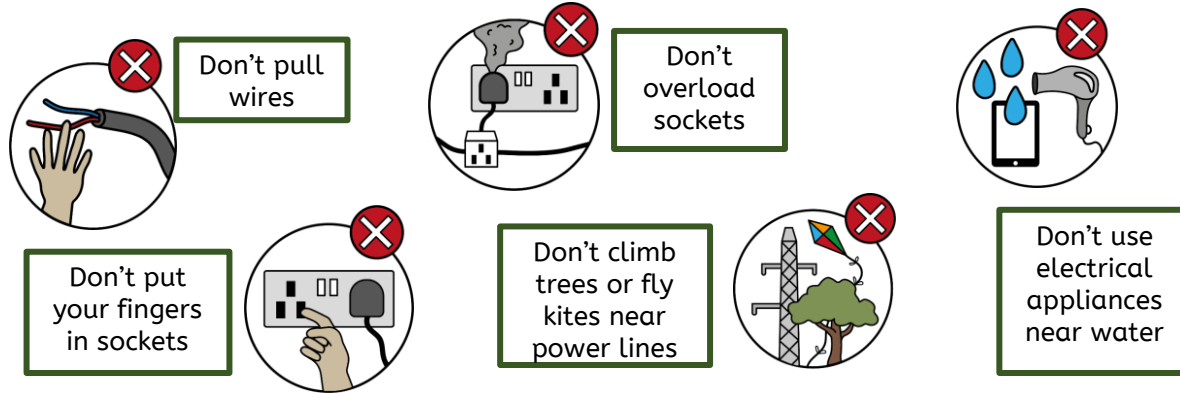


# Electricity

## Electrical safety

It is important to be safe when working with electricity.





## Complete circuits


A complete circuit must have:

- at least one cell
- At least one component
- have all the **components** connected in a loop.

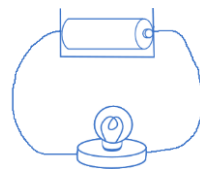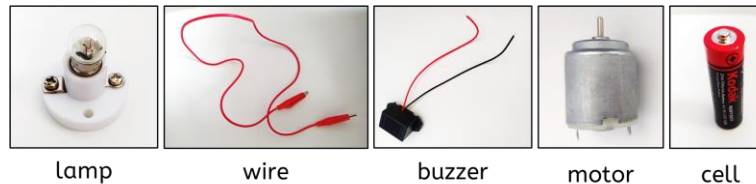If any of these things are missing it is an **incomplete circuit**.



A complete circuit.

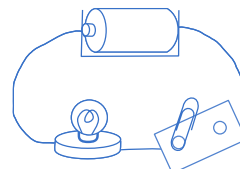

A switch can be used to create a break in a circuit.

## Key vocabulary

- **electrical appliance/device:** something that needs electricity to work. a kettle is an electrical appliance. it uses electricity to heat up a metal wire that then boils the water.
- **electrical circuit:** a path that electricity can flow through. the path must be a complete loop (complete circuit) for the components to work.
- **incomplete circuit:** a loop that is *not* complete. electricity cannot flow through, so the components in the circuit will not work.

## Conductors and insulators

- Materials that let electricity pass through them easily are known as good **electrical conductors**.
- Copper, iron, steel are good conductors.
- **Electrical insulators** do not allow electricity to pass through them easily. They are poor electrical conductors.
- Wood, plastic, rubber and air are good insulators.